

**DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE**

**Regular Winter Examination – 2025**

**Course: (Computer Science and Engineering)**

**Semester: III**

**Subject Code & Name: 25AF1928MD306, Electronic Devices & Circuits.**

**Course Code: 11242**

**Max Marks: 60**

**Date: 09/02/26**

**Duration: 3 Hr.**

**Instructions to the Students:**

1. Each question carries 12 marks.
2. Question No. 1 will be compulsory and include objective-type questions.
3. Candidates are required to attempt any four questions from Question No. 2 to Question No. 6.
4. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in ( ) in front of the question.
5. Use of non-programmable scientific calculators is allowed.
6. Assume suitable data wherever necessary and mention it clearly.

				(Level/CO)	Marks	
<b>Q. 1</b>	<b>Objective type questions. (Compulsory Question)</b>					<b>12</b>
1	In a BJT operating in the active region, the base–emitter junction is				CO1	1
	a) Reverse biased and collector–base forward biased	b) Forward biased and collector–base reverse biased	c) Both junctions reverse biased	d) Both junctions forward biased		
2	The stability factor of a transistor biasing circuit indicates its sensitivity to				CO1	1
	a) Base current	b) Collector current	c) Temperature variation	d) Supply voltage variation		
3	Which transistor configuration provides high current gain and moderate voltage gain?				CO1	1
	a) Common Base	b) Common Emitter	c) Common Collector	d) Emitter Follower		

4	Pinch-off voltage in a JFET is the drain voltage at which				CO2	1
	a) Drain current becomes zero	b) Channel is completely closed	c) Drain current becomes constant	d) Gate current increases sharply		
5	Which FET configuration offers high input impedance and low output impedance?				CO2	1
	a) Common Source	b) Common Drain	c) Common Gate	d) Source Follower		
6	An enhancement-type MOSFET operates only when				CO2	1
	a) $V_{GS} = 0$	b) $V_{GS}$ is negative	c) $V_{GS}$ exceeds threshold voltage	d) $V_{DS}$ is zero		
7	The ideal input impedance of an operational amplifier is				CO3	1
	a) Zero	b) Very low	c) Infinite	d) Equal to output impedance		
8	The main purpose of a differential amplifier in an op-amp is to				CO3	1
	a) Amplify AC signals	b) Amplify DC signals	c) Amplify the difference between two inputs	d) Increase output power		
9	Which IC is commonly used as a general-purpose operational amplifier?				CO4	1
	a) IC 555	b) IC 741	c) IC 4046	d) IC 7400		
10	An op-amp integrator produces an output proportional to				CO4	1

	a) Input voltage	b) Input current	c) Integral of input voltage	d) Derivative of input voltage		
11	An active low-pass filter allows				CO5	1
	a) Only high frequencies	b) Only low frequencies	c) Only mid frequencies	d) All frequencies		
12	The main function of a Phase Locked Loop (PLL) is to				CO5	1
	a) Amplify signals	b) Generate noise	c) Track and lock input frequency	d) Rectify AC signals		
<b>Q. 2</b>	<b>Solve the following.</b>					12
<b>A)</b>	Explain working of BJT in Common Emitter Configuration. Explain what is $\beta$				CO1	6
<b>B)</b>	Explain transistor configurations (CB, CE, CC). Compare them in terms of current gain, voltage gain, input impedance, and output impedance.				CO1	6
<b>Q.3</b>	<b>Solve the following.</b>					12
<b>A)</b>	Explain the construction, operation, and static characteristics of a JFET. Define pinch-off voltage.				CO2	6
<b>B)</b>	Explain the construction and operation of an n-channel enhancement MOSFET. Draw and explain its output characteristics.				CO2	6
<b>Q. 4</b>	<b>Solve Any Two of the following.</b>					12
<b>A)</b>	Draw and explain the block diagram of an operational amplifier. Mention the function of each block.				CO3	6
<b>B)</b>	An inverting amplifier uses an op-amp with an input resistance $R_i = 5 \text{ k}\Omega$ and feedback resistance $R_f = 50 \text{ k}\Omega$ . Determine the voltage gain of the amplifier. If the input voltage is 0.2 V, calculate the output voltage.				CO3	6
<b>C)</b>	Explain the inverting and non-inverting amplifier configurations using op-amp with expressions for voltage gain.				CO3	6

<b>Q.5</b>	<b>Solve Any Two of the following.</b>		12
<b>A)</b>	An op-amp integrator has a resistor $R = 100 \text{ k}\Omega$ and capacitor $C = 0.1 \text{ }\mu\text{F}$ . Find the output voltage when a DC input of 2 V is applied for 0.5 seconds. Assume the initial output voltage is zero.	CO4	6
<b>B)</b>	Draw the circuit diagram of inverting summing amplifier using IC 741 and derive the expression for output voltage.	CO4	6
<b>C)</b>	Explain the operation of a Schmitt trigger using op-amp , defining hysteresis and threshold levels. Mention its applications.	CO4	6
<b>Q. 6</b>	<b>Solve Any Two of the following.</b>		12
<b>A)</b>	Design an active low-pass filter with a cut-off frequency of 1 kHz .Explain the role of op-amp and RC network.	CO5	6
<b>B)</b>	Describe the band-pass and band-stop active filters with neat diagrams and frequency response.	CO5	6
<b>C)</b>	Draw and explain the block diagram of Phase Locked Loop (PLL) and describe its working principle.	CO5	6
<b>*** End ***</b>			